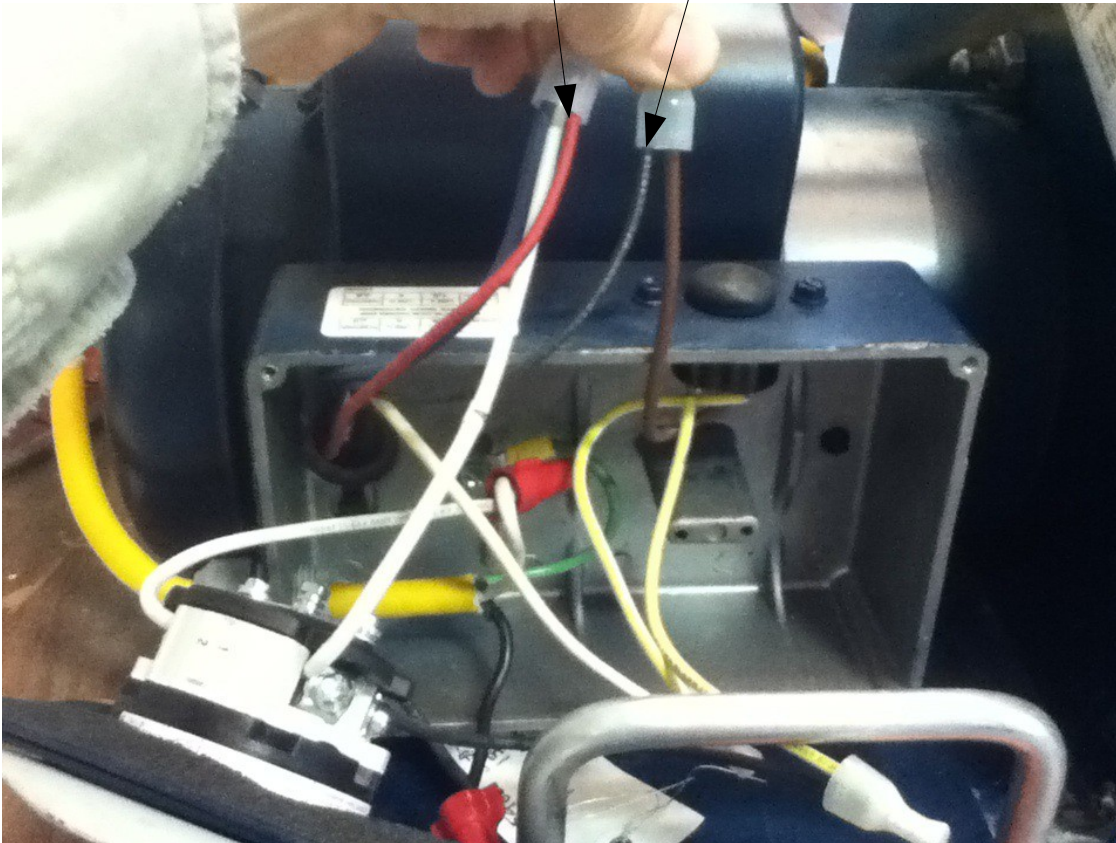


Reversing the direction of the 3HP Baldor motor

Swap 8 (red) and 5 (black)



This picture shows the wiring for the clock-wise “spins to the right” direction.

To reverse the motor, simply swap the red wire, marked with the number 8, and the black wire, marked as number 5.

The final result will have wires A (white), 1 (blue), and 5 (black) together in one wire nut. The other wire nut will have 8 (red) and “J” (brown).